 


Function Simplification

- # Goal: find an equivalent function with the minimum number of literals.

Example: $F(x,y,z) = xyz' + x'yz' + x'y'z' + xy'z'$
 $= yz' + y'z' = z'$

- # Why simplification?
 less hardware,
 same functionality



- # How to simplify functions?

Design Example: An Encoder

- # A 3-input encoder that assigns a 2-bit code to each of the three different input combinations.

- # Don't care conditions.


- # Solutions:

- $a = x'yz' + xy'z' = (x \oplus y)z'$
- $b = x'y'z + xy'z' = (x \oplus z)y'$
- $a = z', b = y'$
- and a lot more

x	y	z	a	b
0	0	1	0	1
0	1	0	1	0
1	0	0	1	1


Where Are the Don't Cares: SDC

 - # **Satisfiability don't cares (SDC)** of a subcircuit/subsystem consist of all input patterns that will never occur.




Where Are the Don't Cares: SDC

 - # **Satisfiability don't cares (SDC)** of a subcircuit/subsystem consist of all input patterns that will never occur.
- # Example: from definition, signal y cannot be 1.




Where Are the Don't Cares: SDC

 - # **Satisfiability don't cares (SDC)** of a subcircuit/subsystem consist of all input patterns that will never occur.
- # Example: for XOR, y input cannot be 1, so $\{x=1, y=1\}$ and $\{x=0, y=1\}$ will be SDCs.



Where Are the Don't Cares: ODC

 - # **Observability don't cares (ODC)** of a subcircuit/subsystem are the input patterns that represent situations when an output is not observed.
- # Example: when $y=0$, output of the XOR cannot be observed. $\{x=1, y=0\}$, $\{x=0, y=0\}$



How Can SDCs and ODCs Help?

- # SDCs: $\{x=1, y=1\}, \{x=0, y=1\}$
- # ODCs: $\{x=1, y=0\}, \{x=0, y=0\}$
- # All the four input combinations are don't care, so the XOR gate can be removed!

