

Hardware Security

-- Digital Logic Design


Cybersecurity Specialization

Outline: Digital Logic Design 101

- # Digital system design/synthesis
 - System specification
 - System implementation
 - Function simplification/optimization
- # Design examples
 - Combinational circuits
 - Sequential system
- # Don't care conditions


Digital Systems

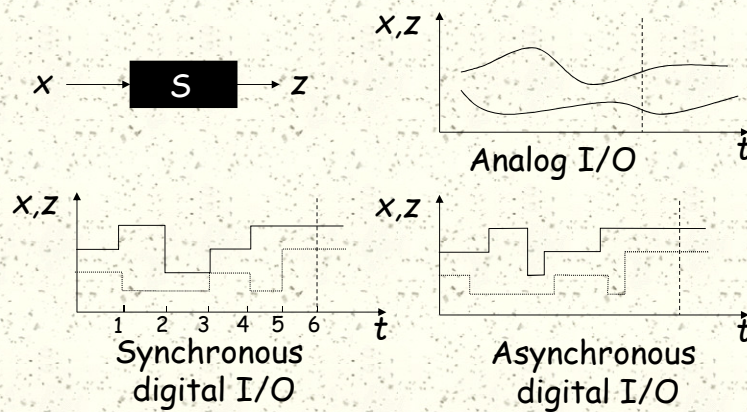- # Digital vs. analog
- # Synchronous vs. asynchronous



Digital Systems

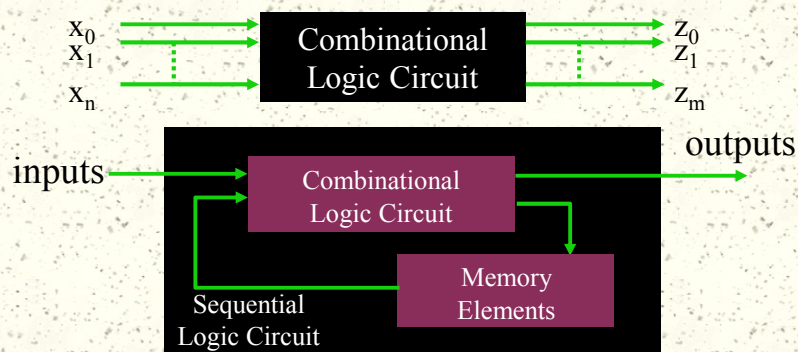- # Digital vs. analog
- # Synchronous vs. asynchronous
- # Combinational vs. sequential



Digital System Specification

- # The **specification** of a system is a description of its functionality and other characteristics required for its use.
- # Developing system specification
 - From high-level to binary-level
 - Input (input signals and current state) encoding
 - Output (output signals and next state) encoding
 - Express output as Boolean functions of input
 - Truth table
 - State transition graph/table

Example: System Specification

- # A system that tells whether a given month has 31 days.
- # High-level system spec:
 - Input: $x \in \{1, 2, 3, 4, 5, 6, 7, 8, 9, 10, 11, 12\}$
 - Output: $z \in \{0, 1\}$
 - Function:
$$z = F(x) = \begin{cases} 0 & x=2, 4, 6, 9, 11 \\ 1 & x=1, 3, 5, 7, 8, 10, 12 \end{cases}$$

x	1	2	3	4	5	6	7	8	9	10	11	12
z	1	0	1	0	1	0	1	1	0	1	0	1

Example: System Spec

A system that tells whether a given month has 31 days.

Binary-level system spec:

■ Input variables/bits: x_3, x_2, x_1, x_0

■ Output variable/bit: z

■ Function:

$$z(x_3, x_2, x_1, x_0) = x'_3 x_0 + x_3 x'_0$$

x	$x_3x_2x_1x_0$	z
1	0 0 0 1	1
2	0 0 1 0	0
3	0 0 1 1	1
4	0 1 0 0	0
5	0 1 0 1	1
6	0 1 1 0	0
7	0 1 1 1	1
8	1 0 0 0	1
9	1 0 0 1	0
10	1 0 1 0	1
11	1 0 1 1	0
12	1 1 0 0	1