

Hardware Security

-- Hardware Trojan and Trusted ICs

Cybersecurity Specialization

What Do We Expect to Learn?

- # Hardware Trojan (HT)
 - What is hardware Trojan
 - Hardware Trojan taxonomy
 - Hardware Trojan detection
- # Trusted integrated circuits (ICs)
 - What are trusted ICs
 - Building trust: HT prevention methods
- # Background
 - You are good since you are here!

What is Hardware Trojan?

- # Hardware Trojan (HT): any addition or modification to a circuit or a system with malicious intention.
- # Characteristics of HT:
 - Malicious goals
 - Change or control functionality
 - Leak sensitive information
 - Reduce circuit reliability
 - Intentional addition/modification

Trusted Integrated Circuits

- # Trusted integrated circuits (IC): an IC does exactly what it is asked for, no more and no less.
- # Examples of untrusted ICs
 - Fail to deliver certain required functionality
 - Have hardware Trojan inside the chip/system
- # Does such trusted IC exist?
- # My definition of trusted IC
 - No less
 - No malicious more


Example of Trusted IC and HT

- # Alice asks Bob to design a circuit that computes $F(x)$ so she can authenticate the $(x, F(x))$ pairs as (username, password).

Assume that $F(x) = x^2$ for $x = 0, 1, 2, \dots, 9$.

- # Bob's design:

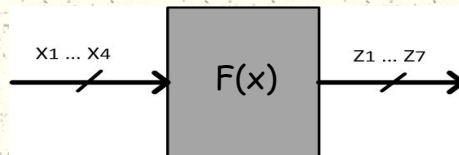- Input: $\{x_1, x_2, x_3, x_4\}$ (e.g. 0: 0000, 3: 0011)
- Output: $\{z_1, z_2, z_3, z_4, z_5, z_6, z_7\}$ (e.g. 81: 1010001)
- Functionality: $z = F(x) = x^2$




The Exact Design Requirements


x_1	x_2	x_3	x_4	x	x^2	z_1	z_2	z_3	z_4	z_5	z_6	z_7
0	0	0	0	0	0	0	0	0	0	0	0	0
0	0	0	1	1	1	0	0	0	0	0	0	1
0	0	1	0	2	4	0	0	0	0	1	0	0
0	0	1	1	3	9	0	0	0	1	0	0	1
0	1	0	0	4	16	0	0	1	0	0	0	0
0	1	0	1	5	25	0	0	1	1	0	0	1
0	1	1	0	6	36	0	1	0	0	1	0	0
0	1	1	1	7	49	0	1	1	0	0	0	1
1	0	0	0	8	64	1	0	0	0	0	0	0
1	0	0	1	9	81	1	0	1	0	0	0	1

Hint: some early quiz question ☺

What is Inside the Design?

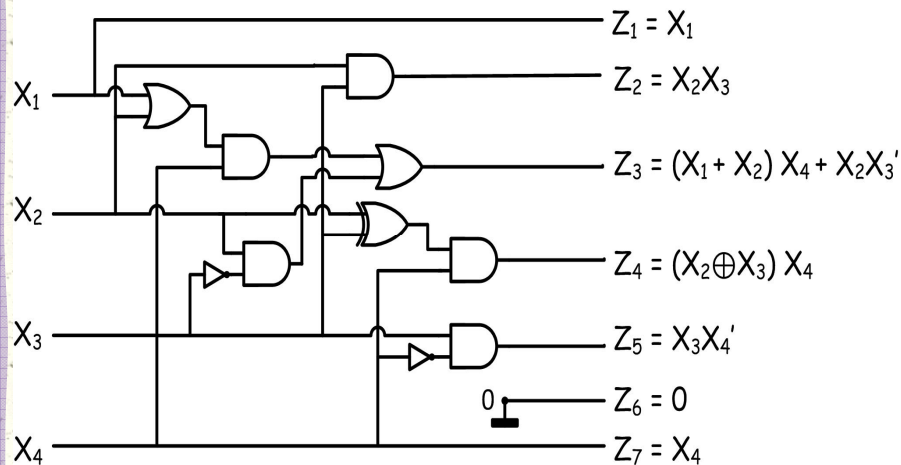

What is Inside the Design?

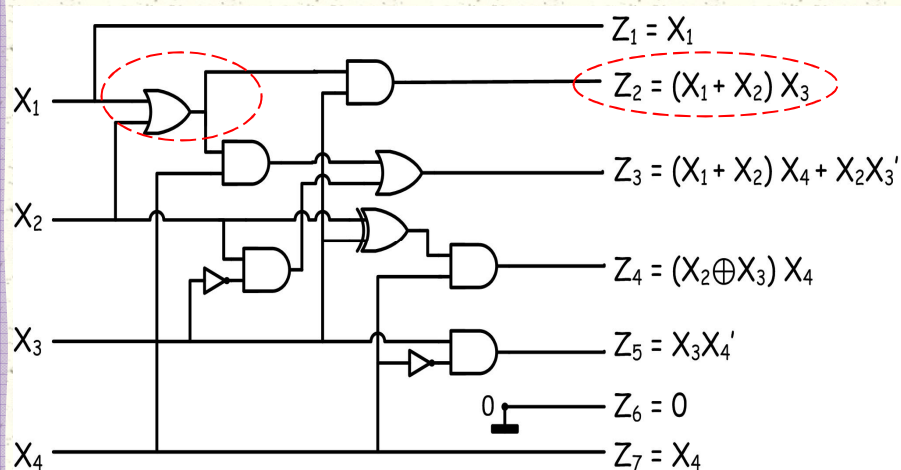

Same number (and type) of gates

Almost identical layout

What More Does the Design Do?

- # $Z_1 = X_1$
- # $Z_2 = (X_1 + X_2) X_3$
- # $Z_3 = (X_1 + X_2) X_4 + X_2 X_3'$
- # $Z_4 = (X_2 \oplus X_3) X_4$
- # $Z_5 = X_3 X_4'$
- # $Z_6 = 0$
- # $Z_7 = X_4$

X_1	X_2	X_3	X_4	X	$F(X)$	Z_1	Z_2	Z_3	Z_4	Z_5	Z_6	Z_7
1	0	1	0	10	68	1	0	0	0	1	0	0
1	0	1	1	11	89	1	0	1	1	0	0	1

X_1	X_2	X_3	X_4	X	$F(X)$	Z_1	Z_2	Z_3	Z_4	Z_5	Z_6	Z_7
1	0	1	0	10	100	1	1	0	0	1	0	0
1	0	1	1	11	121	1	1	1	1	0	0	1

- # (10,100) and (11, 121) become valid!

Hardware Trojan and Trusted IC

- # Hardware Trojan
 - Intentional addition or modification
 - Malicious purpose
- # Trusted IC
 - no less
 - no malicious more
- # Trusted IC must be Trojan-free
- # Assess trust: HT detection
- # Build trust: HT prevention