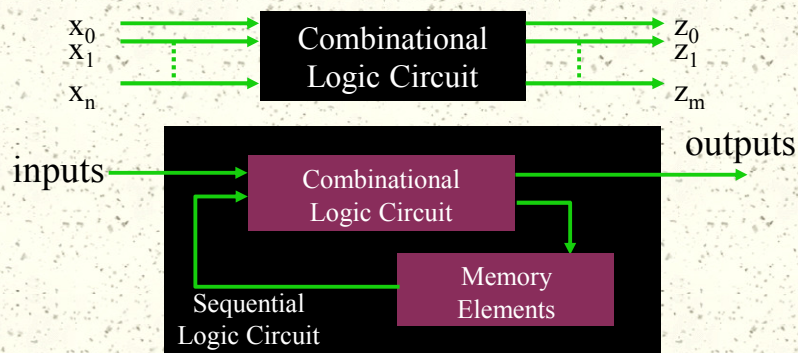



Digital Systems

- # Digital vs. analog
- # Synchronous vs. asynchronous
- # Combinational vs. sequential



Latch: Basic Memory Unit

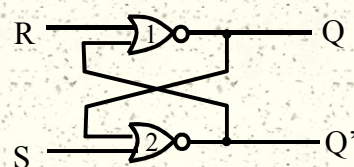- # Two outputs (Q and Q')
- # Various ways to feed latches
- # NOR Gate latch




S	R	Q	Q'
1	0	1	0
0	0	1	0
0	1	0	1
0	0	0	1

- # Outputs of latches may change at any time when input changes (asynchronous system)

Flip-Flop: Basic Memory Unit

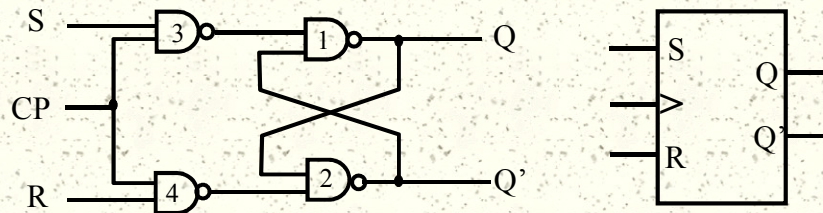- Flip-Flops are similar to latches, but have a signal to control when output will change.



- Three inputs: S, R, CP ($RS = 0$)
- One bit information: $Q(t)$
 - $Q(t+1) = S + R'Q(t)$

Flip-Flop Excitation Tables

- How to feed the FF input line(s) to make its memory change as required.

$Q(t)$	$Q(t+1)$	S	R
0	0	0	x
0	1	1	0
1	0	0	1
1	1	x	0

$Q(t)$	$Q(t+1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

$Q(t)$	$Q(t+1)$	J	K
0	0	0	x
0	1	1	x
1	0	x	1
1	1	x	0

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

Example: System Specification

Design a circuit with one input x and three outputs A, B, C . An external source feeds x one bit per clock cycle, when $x=0$, the outputs remain no change; otherwise, they repeat the binary sequence: 0,1,3,7,6,4, one at a time.

current state			next state					
			$x=0$			$x=1$		
A	B	C	A	B	C	A	B	C
0	0	0	0	0	0	0	0	1
0	0	1	0	0	1	0	1	1
0	1	1	0	1	1	1	1	1
1	1	1	1	1	1	1	1	0
1	1	0	1	1	0	1	0	0
1	0	0	1	0	0	0	0	0

state transition table/graph

